

EE240B Project: Checkpoint 1 & 2

[See our Github repo](#)

Harrison Liew & Vighnesh Iyer

April 8, 2019

Contents

| | | |
|----------|--|-----------|
| 1 | Checkpoint 1: System-Level Design | 2 |
| 1.0 | Top-Level Specs | 2 |
| 1.1 | Filter Type Selection | 2 |
| 1.2 | Filter Topology Selection | 4 |
| 1.3 | Op-Amp or OTA? | 5 |
| 1.4 | Spec Out OTA Stages | 6 |
| 1.5 | Resistor Sizing and Noise Analysis | 7 |
| 1.6 | Power Estimation | 8 |
| 1.7 | Chosen Design Parameters | 9 |
| 2 | Checkpoint 2: OTA Design | 9 |
| 2.1 | Schematic Design | 9 |
| 2.2 | Testbench | 13 |
| 2.3 | OTA Stability | 15 |
| 2.4 | Noise | 15 |
| 2.5 | Comparison with Ideal | 15 |
| 3 | References | 21 |

1 Checkpoint 1: System-Level Design

1.0 Top-Level Specs

To begin, we transcribe the specs given in the project description into a more formal form to reference later.

$$\omega_{pass} = 20 \text{ Mhz} \quad (1)$$

$$A_{v,dc} = 0 \text{ dB} \quad (1)$$

$$A_v(\omega_{pass}) \geq -3 \text{ dB} \quad (1)$$

$$\omega_{stop} = 200 \text{ Mhz} \quad (2)$$

$$A_v(\omega_{stop}) \leq -55 \text{ dB} \quad (2)$$

$$\text{Group Delay} = \tau_g(\omega) = \frac{d\angle H(j\omega)}{d\omega} \quad (3)$$

$$[\max(\tau_g(\omega)) - \min(\tau_g(\omega))] \Big|_{\omega=0}^{\omega=\omega_{pass}} \leq 3 \text{ ns} \quad (3)$$

$$\text{Dynamic Range} = DR = \frac{P_{sig,max} + P_{noise}(s)}{P_{noise}(s)} \Big|_{\omega=1.2\pi}^{\omega=\omega_{pass}} \geq 50 \text{ dB} \quad (4)$$

$$C_{load} = 40 \text{ fF} \quad (5)$$

$$V_{dd} = 1.2 \text{ V} \quad (6)$$

$$\text{minimize}(P_{static}) \quad (7)$$

$$\text{Passband Ripple} = Rip_{max} \leq 1 \text{ dB} \quad (8)$$

$$\text{Stable when driven by a 200mV differential step} \quad (9)$$

1.0.1 Methodology

We approached this design problem with a generator-centric methodology. As an even higher-level than using BAG, we incorporate open-source tools based in Python. First, filter transfer functions are synthesized `scipy` and the given filter specs. Concurrently, a real model of the active filter is generated using `ahkab`, which also synthesizes symbolic transfer functions that include OTA nonidealities. We quickly fit the synthesized filter to the circuit topology using naive design equations, and then use a optimizer to refit the filter resistance and capacitance after adjusting for real non-idealities extracted from transistor-level characterization. After constraining the space of design parameters, we verify that the noise and power meet specifications, and iterate as necessary.

1.1 Filter Type Selection

Given the gain and passband spec 1, the stopband spec 2, and the group delay spec 3, we can synthesize transfer functions for various filter types that minimally meet these specs (in terms of order and extension of passband frequency). We perform this iterative synthesis using the `scipy` Python library.

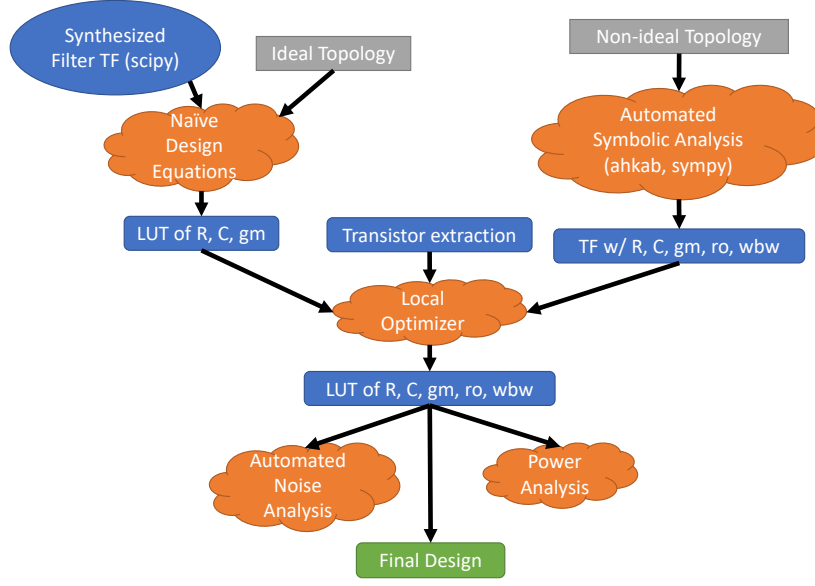


Figure 1: The flow to go from filter specs to a system-level design with parameterized blocks

Algorithm 1 Filter TF Synthesis

```

1: procedure SYNTHESIZE $TF(\omega_{pass}, \omega_{stop}, A_v(\omega_{stop}), Rip_{max}, \tau_{g,max})$ 
2:    $O \leftarrow 1$ 
3:    $\omega_{pass,i} \leftarrow \omega_{pass}$ 
4:   while True do
5:      $BA \leftarrow \text{SCIPY.IIRFILTER}(N \leftarrow O, Wn \leftarrow \omega_{pass,i}, rp \leftarrow Rip_{max}, rs \leftarrow A_v(\omega_{stop}))$ 
6:     if  $A_v(BA, \omega_{stop}) < A_v(\omega_{stop})$  then
7:        $O \leftarrow O + 1$   $\triangleright$  Increase the filter order if stopband attenuation spec isn't met
8:     else if  $A_v(BA, \omega_{pass}) < -3 \text{ dB}$  then
9:        $\omega_{pass,i} \leftarrow \omega_{pass,i} + 1 \text{ Mhz}$   $\triangleright$  Bump the passband corner if there's too much
       attenuation
10:    else if  $\text{Passband Variation}(\tau_{g,BA}) > \tau_{g,max}$  then
11:       $\omega_{pass,i} \leftarrow \omega_{pass,i} + 1 \text{ Mhz}$   $\triangleright$  Bump the passband corner if the group delay variation
       is excessive
12:    else
13:      return  $BA$ 

```

This procedure returns a filter transfer function. Using this technique we can find optimal filter polynomial coefficients BA for each filter type. We plot the transfer functions' magnitude gain (Figure 2) and group delay (Figure 3) over frequency to show they meet the specs.

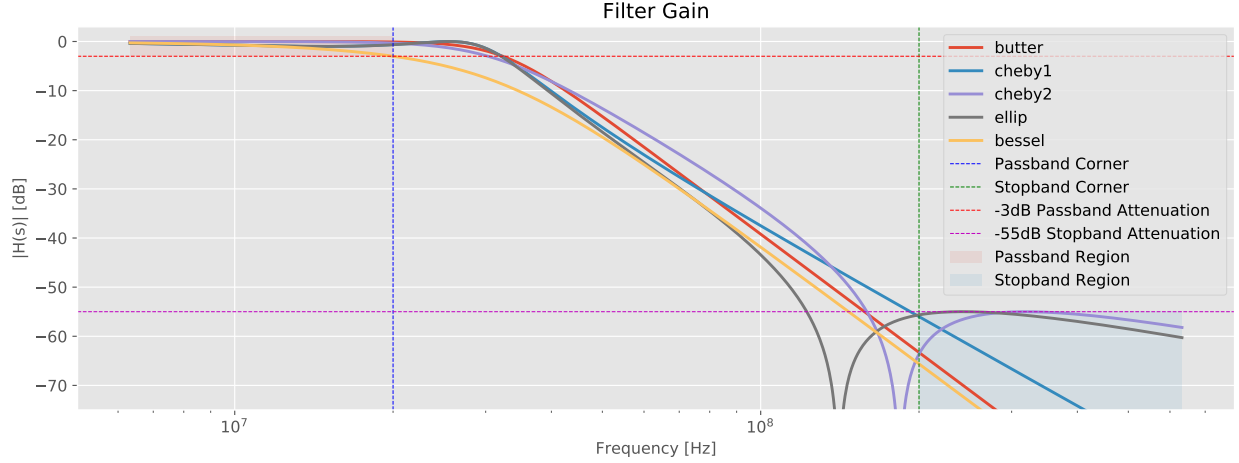


Figure 2: Magnitude gain for synthesized filter transfer functions

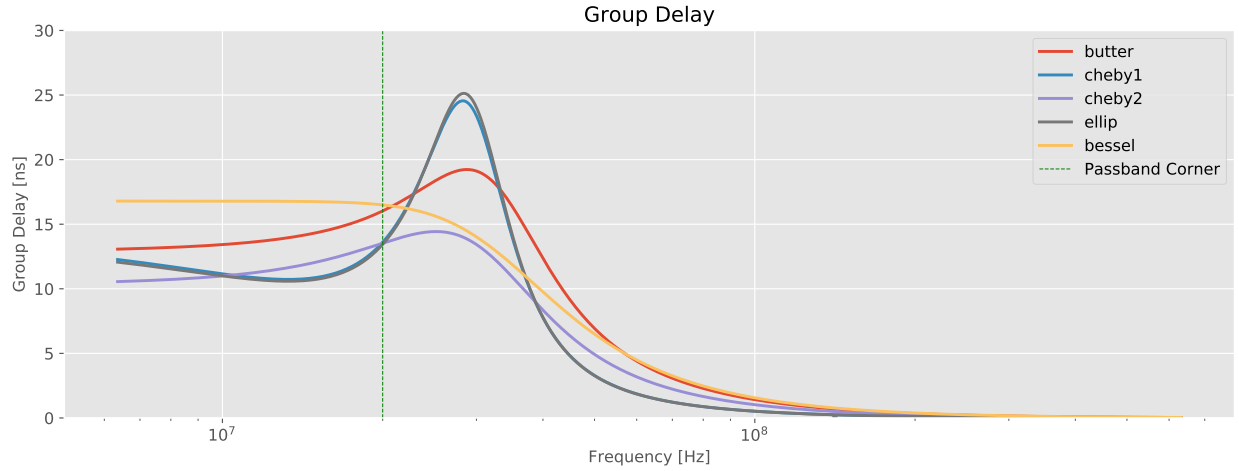


Figure 3: Group delay for synthesized filter transfer functions

We believe the *Butterworth filter* with order = 4 best fits the specifications and is the easiest to design for because the passband frequency needs to be minimally pushed out to achieve the group delay spec and contains no zeros in the transfer function. The *Bessel filter* can also work, but may need to be redesigned to push forward the passband corner for the real design to not exceed -3dB attenuation at the corner frequency.

The other filter types either have zeros in the transfer function or have too much group delay variation forcing the passband corner too far up. They have the advantage of only needing an order = 3, but odd orders don't simplify the circuit topology anyways.

1.2 Filter Topology Selection

We initially considered the Sallen-Key and Multiple Feedback topologies using op-amps since they are straightforward to implement and cascading 2 stages will give us 4 poles as desired.

Later, we switched to using OTAs and decided on this simple 2 pole lowpass topology:

 


Figure 4: OTA-based lowpass filter with 2 poles and 3 passives, assuming the OTA's $R_{out} = \infty$. The output is taken from the top of C_1

The transfer function is:

$$H_{ideal}(s) = \frac{g_m g_1}{s^2 C_1 C_2 + s g_1 (C_1 + C_2) + g_m g_1}$$

The standard design equations are:

$$\omega_o = \sqrt{\frac{g_m g_1}{C_1 C_2}}$$

$$Q = \sqrt{\frac{g_m}{g_1} \frac{\sqrt{C_1 C_2}}{C_1 + C_2}}$$

Now assuming $C_1 = C_2 = C$, we can spec g_1 and g_m :

$$g_1 = \frac{\omega_o C}{2Q}$$

$$g_m = 2Q \omega_o C$$

Since we are using a Butterworth filter, we set $Q = 1/\sqrt{2}$, and we extract ω_o from the transfer function provided by `scipy`.

These design equations are used to generate a table of (R, C, g_m) design points which will be refined in the next step. The rest of the analysis below considers a single-ended filter; a fully differential filter will to first-order have the same transfer function.

1.3 Op-Amp or OTA?

We initially chose op-amps as the active stage, but later realized that the output stage of op-amps is unnecessary for a filter with a capacitive load and just burns extra current. OTAs are more economical and have enough free variables to support the chosen filter family. We plan to cascade 2 of the lowpass OTA circuits (Figure 4) to form the filter.

1.4 Spec Out OTA Stages

The OTA non-idealities we consider are finite output resistance G_o , limited g_m , and finite bandwidth. We still assume that no DC current flows into the OTA.

$$g_m = \frac{g_{m0}}{1 + s/\omega_{bw}}$$

$$G_o = \frac{1}{R_o}$$

We choose to neglect output capacitance C_o and input capacitance C_i , since the parasitic caps are small compared to the filter capacitors and the parasitic caps can be lumped into the filter caps anyways once two filter stages are cascaded.

The transfer function is modified slightly after accounting for the non-idealities:

$$H_{nonideal}(s, r_o, \omega_{bw}) = \frac{g_{m0}r_o}{\left(-\frac{s}{\omega_{bw}} + 1\right) \left(C^2 R r_o s^2 + C R s + 2C r_o s + \frac{g_{m0}r_o}{-\frac{s}{\omega_{bw}} + 1} + 1.0\right)}$$

The new ω_0 has slightly shifted and the DC gain is now slightly offset from 0 as $\frac{g_{m0}r_o}{1+g_{m0}r_o}$. The Q factor has increased due to the bandwidth restriction of g_m , but comes at the cost of the poles being shifted towards the RHP. Also the finite output resistance greatly influences the passband loss which means either the filter's passband corner should be bumped up or more bias current is needed to boost the g_m .

We take the table of (R, C, g_m) produced by the design equations in the earlier section and resolve for their optimal values given the OTA non-idealities.

To get an idea of the space of transistor non-idealities we will encounter, we extracted transistor parameters from HW#1. Since most of the design parameters are dependent on the input differential pair, we want to bound all the relevant transistor specs for a variety of transistor bias points. By simulating a L=135nm and W=150nm NMOS over a range of bias current, we grab about 20 bias points (for V^* ranging from 0.1 to 0.5V) and generate a LUT containing parameters such as $g_m, r_o, \omega_{bw}, I_d$, and V^* , all of which will be used for adjusting the optimizer and calculating noise and power.

With a table of realizable r_o and ω_{bw} values, we run a local optimizer which attempts to fit the non-ideal $H(s)$ to the ideal-case $H(s)$.

$$\min_{R, C, g_{m0}} \|H_{ideal}(s) - H_{nonideal}(s, r_o, \omega_{bw})\|_2^2 \Big|_{s=\omega_{pass}-\epsilon}^{s=\omega_{stop}+\epsilon}$$

The initial guess of R and C is provided by the table from section 1.2 and the local optimizer figures out how these variables should be adjusted.

As an example, for these specific non-ideality values and initial guesses for R, C :

$$\begin{aligned} A_{v0} &= 20 \text{ V/V} \\ \omega_{bw} &= 25.3 \text{ GHz} \\ g_{m0} &= 0.744 \text{ mS} \\ R &= 6 \text{ k}\Omega \\ C &= 1.32 \text{ pF} \end{aligned}$$

We get these modifications of R, C, g_{m0} after optimization:

$$\begin{aligned} R' &= 3.23 \text{ k}\Omega \\ C' &= 2.82 \text{ pF} \end{aligned}$$

1.5 Resistor Sizing and Noise Analysis

For a single OTA filter stage, we can calculate the output noise of R_1 and the OTA itself (thermal and flicker noise of a g_m cell). In the circuit, we model the resistor and OTA's noise as noise currents, for which we calculate a symbolic transfer function for the input-referred noise voltage. In this analysis, we can neglect the OTA's finite bandwidth, as it is too high to shape noise in the passband. We also make the assumption that cascode devices in the OTA do not contribute any noise, and current source/CMFB circuits do not contribute any differential noise.

$$\begin{aligned} H_{ni,R}(s) &= \frac{R(sC_2r_o + 1)}{g_m r_o} \\ H_{ni,OTA}(s) &= \frac{1}{g_m} \end{aligned}$$

Intuitively, this makes sense, because R 's current noise at DC (where the caps are AC ground) circulates solely in R , and as the frequency increases past the zero created by C_2 and r_o , noise current flows into the OTA as well and gets amplified. The OTA's noise current is simply input-referred by its own transconductance as expected, and is therefore constant with bias. As the g_m of the OTA is decreased, C_2 increases, so we should expect the filter to be noisier at lower OTA bias.

If we use the following noise currents, setting $\gamma = 2$ for a relatively short channel device, and using the optimized R for a given g_m , we integrate over the passband for one stage:

$$v_{ni,T} = \int_{1\text{Hz}}^{20\text{MHz}} \left[\frac{4kT}{R} |H_{ni,R}(s)|^2 + (4kT\gamma g_m + \frac{K_f I_D}{L^2 C_{ox} f}) |H_{ni,OTA}(s)|^2 \right] df$$

Now if 2 stages are cascaded, we can similarly calculate the total output noise assuming isolation between the two stages. The first stage's R and OTA will have the same input-referred noise, while the second stage's input-referred noise will be attenuated by A_{v0} of the first stage. Since the component values should not change much, and the DC gain is unity, the noise power should be about double that of a single stage.

Taking some values for R and g_m from the previous section, we can calculate the absolute output noise power. With the dynamic range requirement 4, we have a hard limit on this quantity:

$$P_{sig,max} = \frac{V_{sig,max}^2}{2} = \frac{0.2^2}{2} = 0.02W$$

$$P_{ni,max} = \frac{P_{sig,max}}{10^{50/10}} = 200nW$$

We run all the component values in our LUT through this noise calculation to find out which OTA bias points can satisfy the noise spec. We use the following constants in the noise calculations:

$$\begin{aligned}\gamma &= 2 \\ K_f &= 6 \times 10^{-29} \text{ A}^*F \\ L &= 135 \text{ nm} \\ C_{ox} &= 97 \text{ aF}\end{aligned}$$

Figure 5 confirms that at low bias currents, noise is dominated by the filter resistor, and asymptotically approaches the OTA noise at high bias currents. With one stage, we have at least a 20dB margin on the dynamic range. This suggests to us that the choice of bias point is essentially input swing-limited: the V^* must be at least 100mV.

Later on, if we discover that the OTA's noise and nonidealities are much worse than we calculate in this analysis and/or we require additional stages, we can introduce an optimizer once again to adjust all component values at higher OTA bias currents to meet the dynamic range spec.

1.6 Power Estimation

We estimate the static power of the filter circuit as:

$$P = I_{ds} \cdot N_{stages} \cdot N_{branches} \cdot V_{dd} \cdot 2$$

where N_{stages} is 2 representing the number of OTAs, $N_{branches}$ is 2 estimating the number of bias current branches within each OTA, V_{dd} is from the spec, and the factor of 2 accounts for the differential OTA. I_{ds} is derived using 1-transistor simulations and it is collected along with all the OTA non-idealities we considered earlier.

We find the following plot:

All the noise numbers meet our required spec, so we are primarily concerned with getting the required output swing and minimizing distortion. To that end, we can increase V^* and by consequence I_{ds} incrementally until those specs are met without worrying too much about noise.

 


Figure 5: Considering various I_{ds} values for a fixed dimension transistor, we find the total input referred noise and estimated power consumption

1.7 Chosen Design Parameters

Here is one design point which meets our specs:

$$V^* = 0.115 \text{ V}$$

$$I_{ds} = 112 \mu\text{A}$$

$$g_m = 0.195 \text{ mS}$$

$$r_o = 12.7 \text{ k}\Omega$$

$$w_{bw} = 43.3 \text{ GHz}$$

$$R = 12 \text{ k}\Omega$$

$$C = 746.25 \text{ fF}$$

This is the output of our optimization program:

Total input referred noise power: 7.424237673893265e-09 V²

Min reqd voltage swing for DR: 0.0385337194516524 V

Passes dynamic range!

Power: 0.00010751999999999999 W

2 Checkpoint 2: OTA Design

2.1 Schematic Design

2.1.1 Pseudo-Differential Filter

The 3-passive single-ended OTA filter from section 1.2 was modified to form a psuedo-differential filter section as shown in Fig. 6. This filter uses 2 single-ended OTAs, and with ideal OTAs, implements the same transfer function as the single-ended filter designed in checkpoint 1.

 


Figure 6: A single stage of the psuedo-differential OTA filter.

We cascade 2 to 3 of these stages to achieve the required attenuation and group delay specs. This psuedo-differential filter doesn't provide any common mode rejection, but that is solved by using a fully differential OTA in unity gain before the filter stages with the necessary CMRR.

2.1.2 OTA

The single-ended OTA uses a simple telescopic cascoded topology with a cascoded mirror load. Only 1 stage is required to get enough g_m and bandwidth to meet the filter specs. Fig. 7 is the OTA schematic which is sized with these constants:

$$\begin{aligned} I_{bias} &= 50\mu\text{A} \\ L &= 180 \text{ nm} \\ W &= 500 \text{ nm} \\ V_{b,cas,n} &= 1.1 \text{ V} \\ V_{b,cas,p} &= 450 \text{ mV} \end{aligned}$$

With this biasing for all LVT transistors, we achieve $\approx 140\text{mV}$ of V^* in the input pair transistors. Because this is a single stage OTA, the dominant pole is from the mirror, and thus the mirror's sizing relative to the secondary pole at the unloaded output node determines the phase margin. The cascode devices use min. L to reduce parasitic capacitance with a V^* of $\approx 130\text{mV}$. The input pair was most important for meeting the dynamic range spec because noise is dominated by their flicker noise; we chose the minimum area possible while achieving a differential G_m of about $80\mu\text{ S}$. Finally, our R_{out} is approx. $1\text{G}\Omega$, which is high enough to not affect the filter response.

2.1.3 CM Reject Stage

The CMMR reject stage is structurally similar to the OTA to have common output common mode and is shown in Fig. 8. The only differences between the two circuits are:

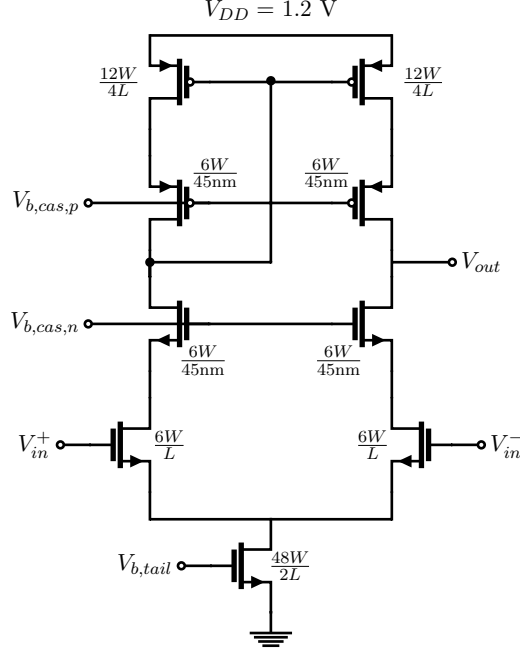


Figure 7: Schematic and sizing of single-ended OTA

- Both loads are diodes, such that $g_{m,p} \approx g_{m,n}$ for unity gain (this was tested across different P/N corners with only 1dB impact on the DC gain). The sizing must be matched with the PMOSs of the OTAs for the common mode to remain equal, as will be explained below.
- The NMOS cascode is moved down above the tail current source to increase the tail's R_{out} , which is the primary contributor to CMRR. The bias voltage is 700mV instead.
- An ideal CMFB circuit senses the desired common mode from a replica OTA, and adjusts the tail current bias as referenced against the gate voltage of a diode sinking the same current as the OTAs.

This stage has the following biases as a result of the different cascode structure:


$$V_{b,cas,n} = 700 \text{ mV}$$

$$V_{b,cas,p} = 450 \text{ mV}$$

$$V_{in,cm} = 900 \text{ mV}$$

2.1.4 Replica Biasing

The DC bias point of each OTA's output and negative terminal is set by the resistive feedback of the filter. However, the DC bias point of the OTA's input needs to be matched with the output common mode bias point of the CMRR stage. To make all common mode voltages equal, we recognize that we can just place a replica OTA with its output and both inputs shorted, thereby creating a structure that has two current mirrors back-to-back as shown in Fig. 9. The resulting

 

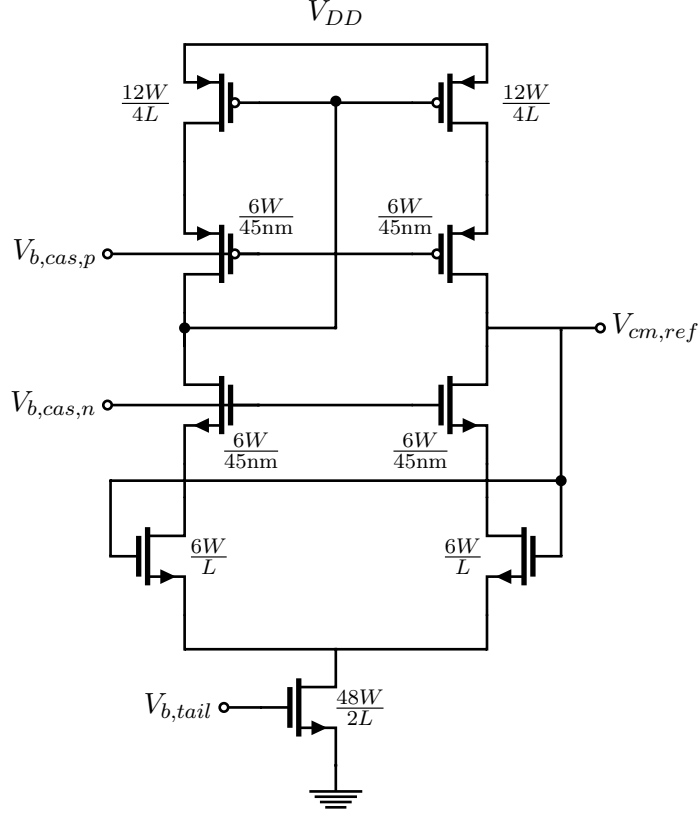


Figure 9: Schematic and sizing of the replica circuit

self-biased voltage feeds the common reference of the CMFB circuit in the CMRR stage. Startup could be an issue, but transient sims show that leakage current prevents the circuit from staying locked in a 0 current state as the supply is quickly or slowly ramped. If certain startup time is required, a small startup circuit could be attached. The sizing of this stage can be made much smaller than the OTAs if common mode noise is not a concern.

2.2 Testbench

Testbenches were made at each stage of the design process, measuring specs such as open loop gain and bandwidth, unity gain step response, and CMRR. Here we describe the system-level testbench as shown conceptually in Fig. 10 and in detail in 11, which contains:

- 2 filter stages, a CMRR stage, and a replica bias circuit for the real filter
- A filter with ideal OTAs
- Ideal current source to mirror to all OTA tail current sources
- Ideal voltage sources for the cascode biases and input common mode
- Ideal balun to convert differential and common-mode components of the stimulus for AC & transient sims

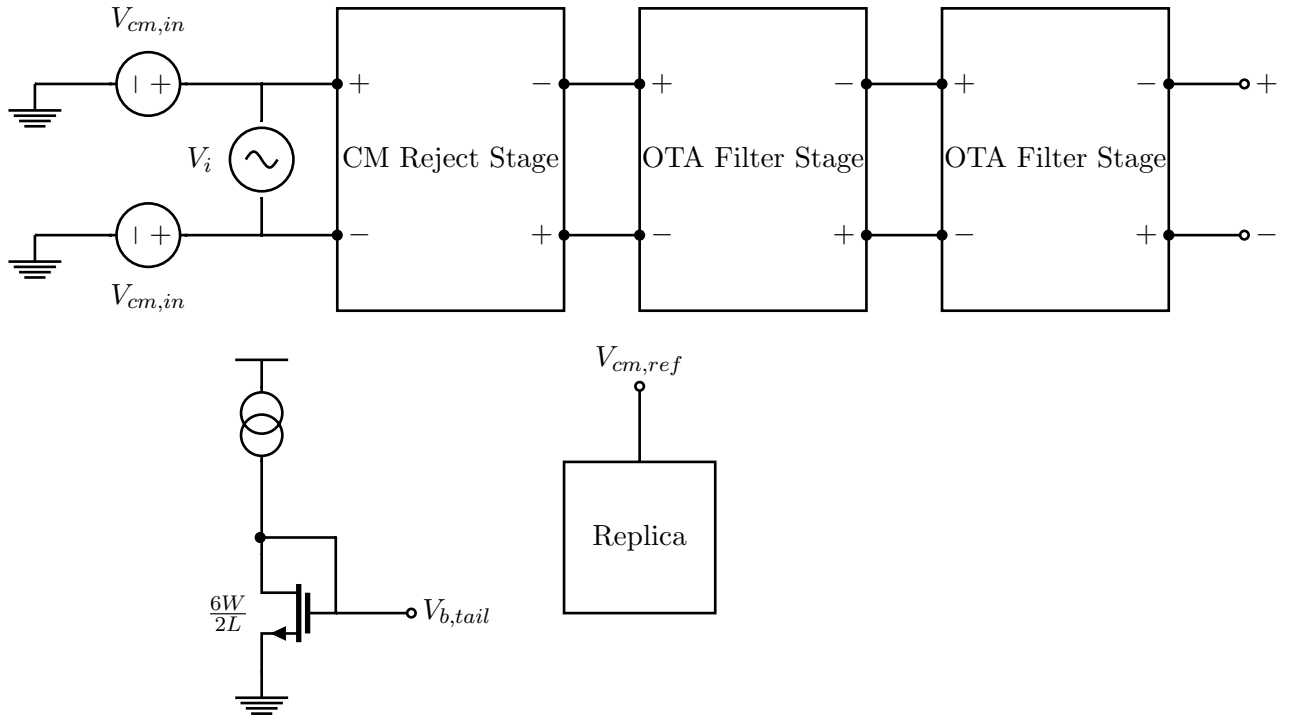


Figure 10: The system-level testbench with bias

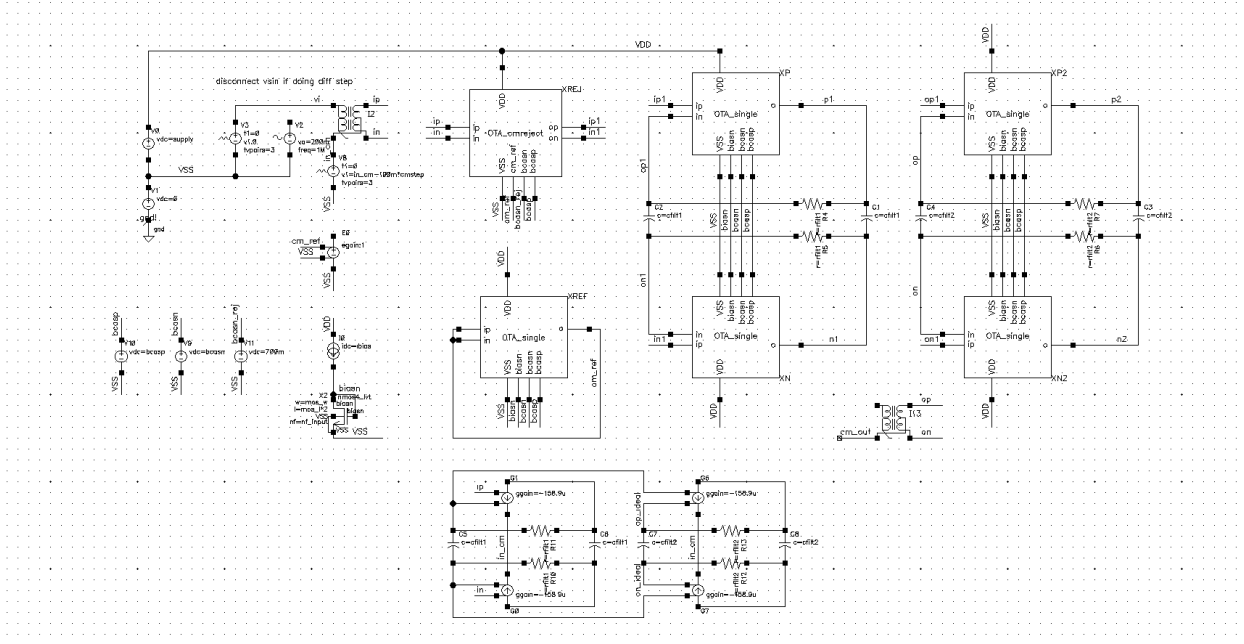


Figure 11: The detailed system-level testbench schematic

 


Figure 12: OTA stability with 200mV differential step

2.3 OTA Stability

The transient simulations on the pseudo-differential OTA in unity gain feedback in response to differential and common-mode steps with rise time of 1ps are shown in Figs. 12 and 13, respectively. Both are demonstrated to be stable, and we must note that the common-mode step is not rejected because the CM rejection is performed by a separate CM reject stage, in front of the filter stages, whose CM step response will be shown later.

Fig. 14 shows that the pseudo-differential OTA in open-loop has a phase margin of about **62 degrees**.

2.4 Noise

Fig. 15 shows the input and output noise density. It is clear that the noise is dominated by flicker noise, and analysis of the noise contributors shows that it comes mostly from the input pair. We sized the W and L of the OTA such that we would meet the dynamic range requirement with the CM reject stage and 3 filter stages.

2.5 Comparison with Ideal

To compare our filter to a filter with an ideal OTA, we note that the CMRR would be infinite and it will be perfectly linear. Thus, we will just show comparisons in the frequency response, differential step settling, and noise.

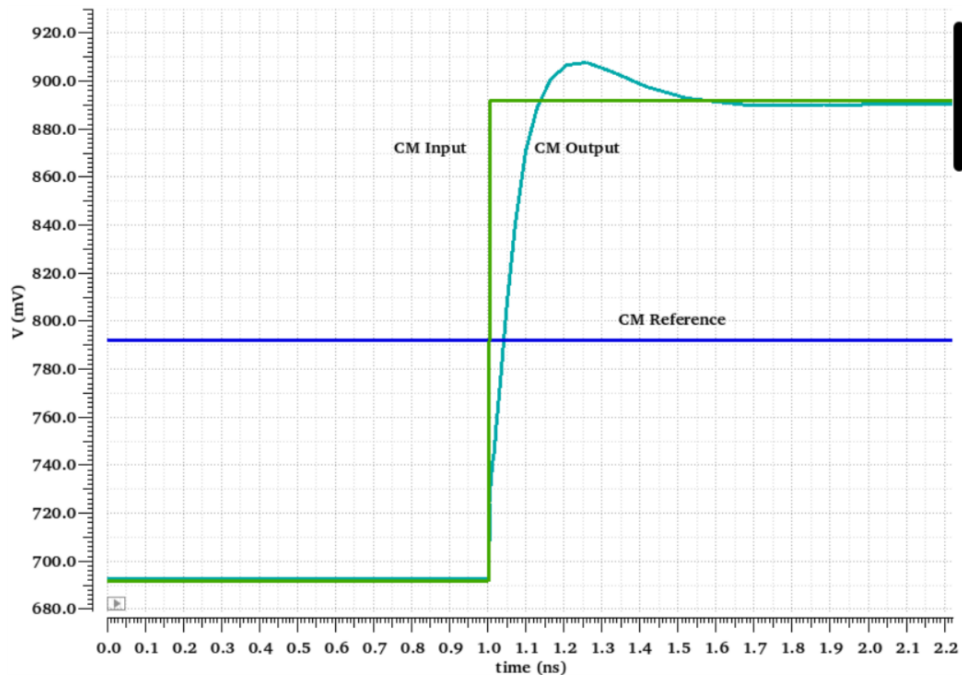


Figure 13: OTA stability with 200mV common-mode step

 


Figure 14: OTA phase margin

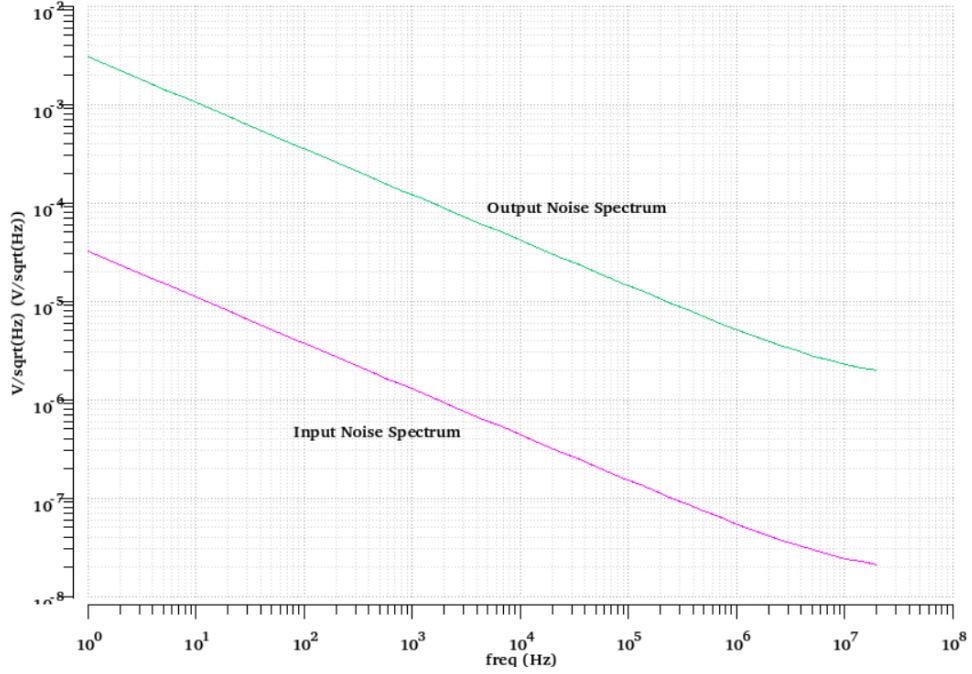


Figure 15: OTA input and output noise spectrum from 1Hz to 20MHz

2.5.1 Filter Passives

To meet the required pole frequency and quality factor, the following filter passives values were chosen:

$$R_{filt,1} = 8.05 \text{ k}\Omega$$

$$C_{filt,1} = 390 \text{ fF}$$

$$R_{filt,2} = 3.4 \text{ k}\Omega$$

$$C_{filt,2} = 670 \text{ fF}$$

2.5.2 Frequency Response

Fig. 16 shows the simulated filter frequency response of our real filter and the filter with the OTA replaced by an ideal VCCS. The transconductance of the ideal OTA is set from the extraction of G_m of our real OTA in open loop simulations. The real filter was tuned to meet both the passband and stopband attenuation specifications with 2 stages at the moment. Due to additional zeros and other parasitic effects, the resulting transfer function looks much closer to a type-II Chebyshev filter than the ideal Bessel. Pole Q's and the corner frequency had to be tuned for the real filter to try to meet the group delay spec (which we still *do not yet* meet - a 3rd filter stage will help), hence why the filter with the ideal OTA does not appear to have a correct corner frequency.

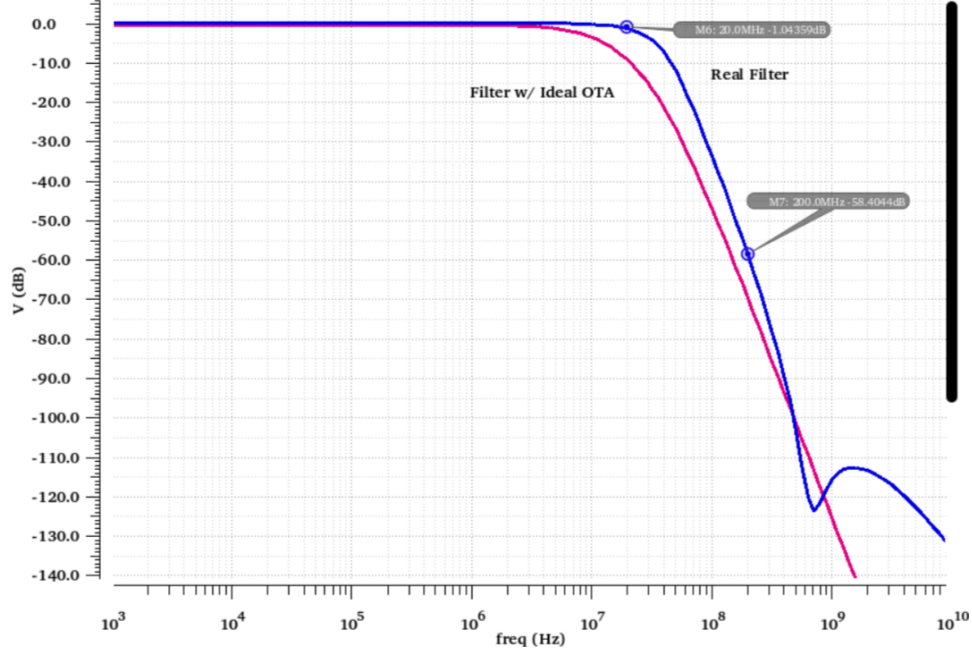


Figure 16: Filter frequency response

2.5.3 Step Response

Figs. 17 and 18 show the response to 200mV differential and common-mode steps with rise time of 1ps. The differential step response is very similar to that of the OTA stages in unity gain feedback, as expected, whereas the filter with ideal OTA has no overshoot because it has infinite bandwidth. Discrepancy in the final output differential voltage is caused by the slight DC gain in our CM rejection amplifier. The first common-mode rejection stage is also stable (albeit with an ideal CMFB circuit). Slight ripple in the common mode is caused by feedthrough in the CMRR stage's input pair due to the 1ps rise time and infinite bandwidth of the ideal CMFB circuit. A real CMFB circuit would show a more realistic CM step response. As long as the CMFB circuit has at least double the bandwidth of the filter itself, we should meet the settling spec. An additional plot of the CMRR over frequency is shown in Fig. 19, and we are currently achieving almost **68dB** of rejection and it remains above 60dB over the entire passband.

2.5.4 Noise

The input referred noise power integrated from 1 to 20MHz is:

- Real filter: **90 nV^2** or **300 μV** differential
- Filter w/ ideal OTA: **2.6 nV^2** or **51.4 μV** differential

The noise of the real filter is **56.6dB** lower than the 200mV differential input that we are expected to receive. Both filter's output noise spectrums are shown in Fig. 20, and once again, we are dominated by flicker noise from the input pairs of all amplifiers in the passband.

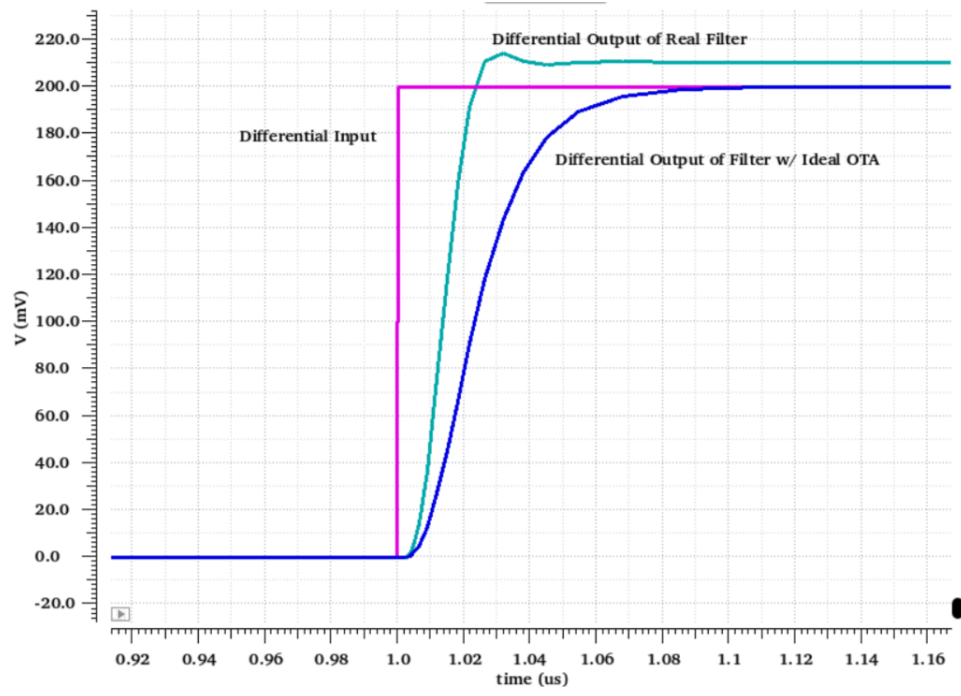


Figure 17: Filter response to 200mV differential step

 


Figure 18: Filter response to 200mV common-mode step

 


Figure 19: Filter CMRR vs. frequency

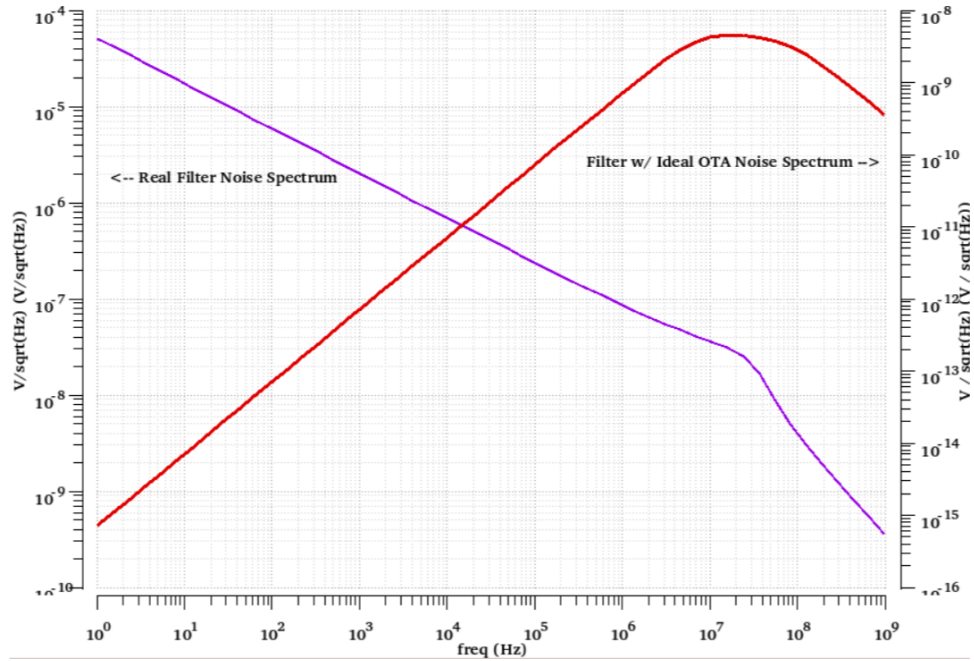


Figure 20: Filter output noise spectrum

2.5.5 Linearity

The linearity for a 200mVpp input at 1MHz is calculated by performing a harmonic balance simulation with 9 harmonics and probing the expression, `drplPssHarmThd((vh('hb "/op") - vh('hb "/on")) 1)`. The balanced structure removed the even-order harmonics as expected, and our bias points leave plenty of headroom on each transistor to accommodate additional input or output swing. The resulting THD = **0.1835%**.

3 References

We found the book, "Continuous-Time Active Filter Design" by T. Deliyannis et al. to be very useful in deriving simple design equations and choosing topologies. [Ahkab](#), a symbolic Python circuit simulator, helped us greatly with more complex calculations such as noise analysis.